

Studi Aliran Daya

(Power Flow Analysis)

Mata Kuliah Analis Sistem Tenaga

Agenda

- Matriks Admitansi
- Persamaan Aliran Daya
- Metode Gaus-Siedell
- Metode Newton-Raphson

> Part 1
> Part 2

Referensi utama : Power System Analys – Hadi Saadat Chapter 6


Pendahuluan

- Studi aliran daya merupakan penentuan/perhitungan tegangan, arus, daya, dan PF yang terdapat pada berbagai simpul dalam suatu jaringan listrik keadaan operasi normal. Hal ini penting untuk perencanaan, pengoperasian, dan perawatan.
- Sistem dalam keadaan seimbang; dengan demikian kita dapat melakukan perhitungan dengan menggunakan model satu-fasa.
- Semua besaran dinyatakan dalam per-unit; dengan demikian berbagai tingkat tegangan dalam sistem sebagai akibat digunakannya transformator, tidaklah menjadi persoalan.

Pendahuluan

Pril 2011

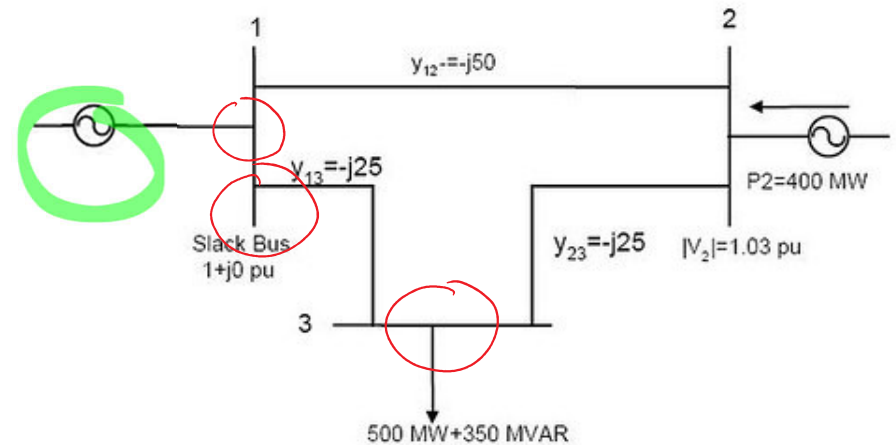- Analisa system tenaga direpresentasikan **permodelan** terhadap komponen-komponen system tenaga seperti **gen, trafo, GI, transmisi, shunt cap, inductor, dan load.**
- Terdapat tiga jenis bus :
 - Generator Bus ✓
 - Load Bus
 - Slack/Swing/Ref Bus



Type of Buses	Know or Specified Quantities	Unknown Quantities or Quantities to be determined.
Generation or P-V Bus	$P, V $	Q, δ → <i>shunt phase</i>
Load or P-Q Bus	P, Q	$ V , \delta$ → <i>shunt phase</i>
Slack or Reference Bus	$ V , \delta$	P, Q

Matriks Admitansi : KCL

$$Y = \frac{1}{Z}$$

Impedansi → Sekecil mungkin
ambat


Admitansi → sekecil mungkin
kecil dan banyak
konduktansi

$$I_2 = Y_{ij} V_j = \frac{1}{Z_{ij}} = \frac{1}{R_{ij} + jX_{ij}}$$

Resistansi Reaktansi

$$I = Y \cdot V$$

kompleks
h-hus

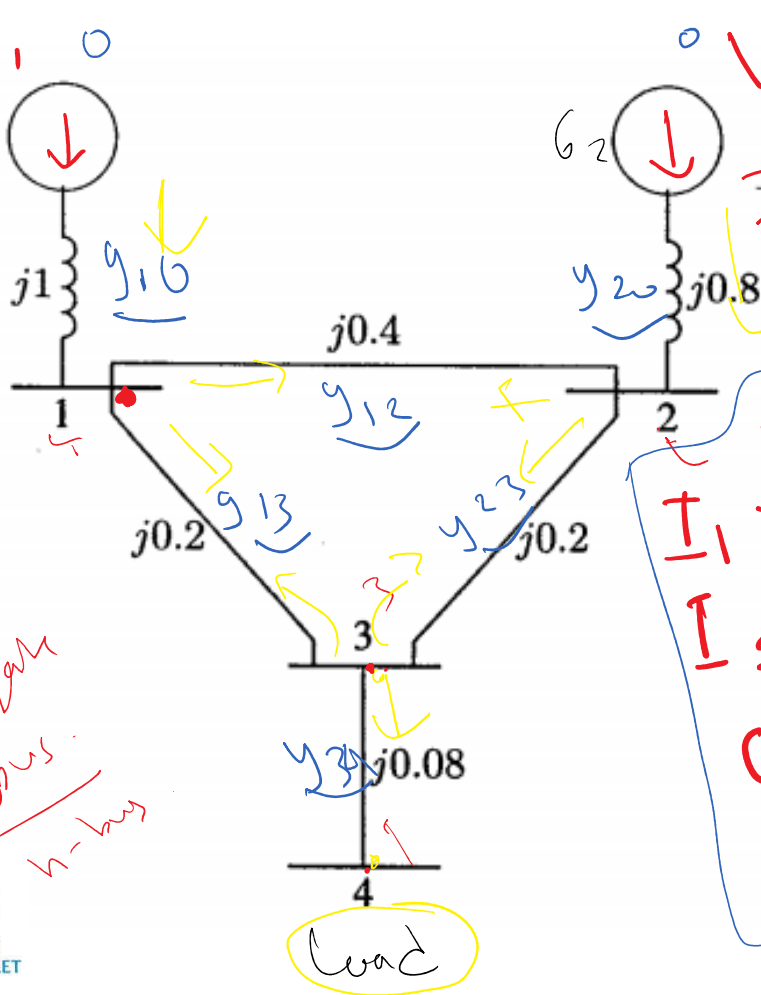

KCL

$$I_1 = Y_{10} V_1 + Y_{12} (V_1 - V_2) + Y_{13} (V_1 - V_3)$$

$$I_2 = Y_{20} V_2 + Y_{12} (V_1 - V_2) + Y_{23} (V_2 - V_3)$$

$$0 = Y_{23} (V_3 - V_2) + Y_{13} (V_3 - V_1) + Y_{34} (V_3 - V_4)$$

$$0 = Y_{34} (V_4 - V_3)$$

$$I_1 = (\underbrace{y_{10} + y_{12} + y_{13}}) V_1 - y_{12} V_2 - y_{13} V_3$$

$$I_2 = -y_{12} V_1 + (\underbrace{y_{20} + y_{12} + y_{23}}) V_2 - y_{23} V_3$$

$$0 = -y_{13} V_1 - y_{23} V_2 + (\underbrace{y_{13} + y_{23} + y_{30}}) V_3 - y_{30} V_4$$

$$0 = -y_{30} V_3 + y_{30} V_4$$

$$Y_{11} = y_{10} + y_{12} + y_{13}$$

$$Y_{22} = y_{20} + y_{12} + y_{23}$$

$$Y_{33} = y_{13} + y_{23} + y_{30}$$

$$Y_{44} = y_{30}$$

$$Y_{12} = Y_{21} = -y_{12}$$

$$Y_{13} = Y_{31} = -y_{13}$$

$$Y_{23} = Y_{32} = -y_{23}$$

$$Y_{34} = Y_{43} = -y_{30}$$

$$I_1 = Y_{11}V_1 + Y_{12}V_2 + Y_{13}V_3 + Y_{14}V_4$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2 + Y_{23}V_3 + Y_{24}V_4 = 0$$

$$I_3 = Y_{31}V_1 + Y_{32}V_2 + Y_{33}V_3 + Y_{34}V_4$$

$$I_4 = Y_{41}V_1 + Y_{42}V_2 + Y_{43}V_3 + Y_{44}V_4$$

$$\begin{bmatrix} I_1 \\ \vdots \\ I_n \end{bmatrix} = \begin{bmatrix} \cdot & \cdot & \cdot & \cdot \\ \cdot & \cdot & \cdot & \cdot \\ \cdot & \cdot & \cdot & \cdot \\ \cdot & \cdot & \cdot & \cdot \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \end{bmatrix}$$

Pengamaan matriksnya :

$$\begin{bmatrix} I_1 \\ I_2 \\ \vdots \\ I_n \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} & \dots & Y_{1n} \\ Y_{21} & Y_{22} & \dots & Y_{2n} \\ \vdots & \vdots & \ddots & \vdots \\ Y_{n1} & Y_{n2} & \dots & Y_{nn} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ \vdots \\ V_n \end{bmatrix}$$




$$\bar{I}_{bus} = \bar{Y}_{bus} \cdot \bar{V}_{bus}$$

$$\bar{V}_{bus} = \bar{Y}_{bus}^{-1} \cdot \bar{I}_{bus}$$

$$\bar{Y}_{bus} = \bar{V}_{bus}^{-1} \cdot \bar{I}_{bus}$$

Contohs administrasi

Power Flow Equation

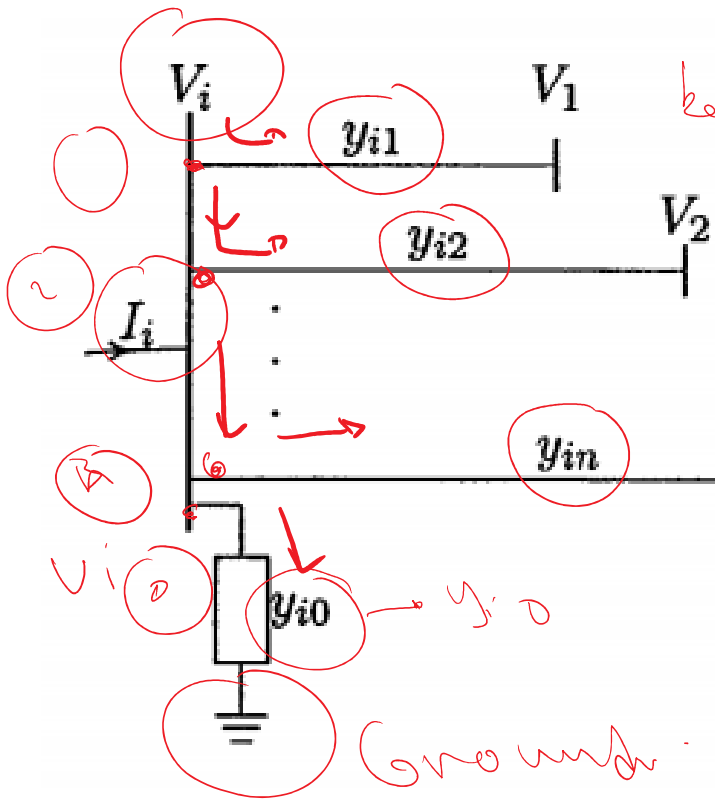

$$\rightarrow I_i = y_{i0} \cdot V_i + y_{i1}(V_i - V_1) + y_{i2}(V_i - V_2) + \dots + y_{in}(V_i - V_n)$$

$$I_i = (y_{i0} + y_{i1} + y_{i2} + \dots + y_{in}) V_i - y_{i1} V_1 - y_{i2} V_2 - \dots - y_{in} V_n$$

$$I_i = V_i \sum_{j=0}^n y_{ij} - \sum_{j \neq i}^n y_{ij} V_j$$

$$S = V_i \cdot I_i^*$$

$$P_i + jQ_i = V_i I_i^*$$

$$I_i = \frac{P_i + jQ_i}{V_i^*}$$

$$\frac{P_i + jQ_i}{V_i^*} = V_i \sum_{j=0}^n y_{ij} - \sum_{j=1}^n y_{ij} V_j$$


Gauss - Seidel
Newton - Raphson
aktif

persamaan
dan iterasi

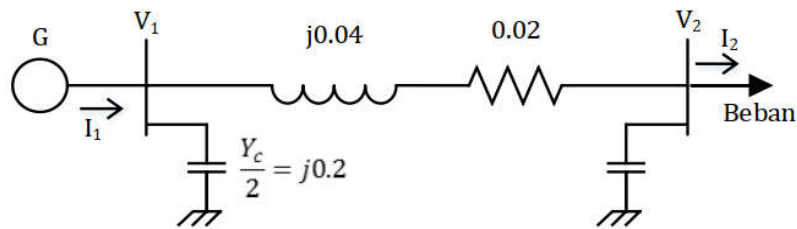Exercise 1.


No. 1

Define the admittance matrix and V_1 , V_2 , If $I_1 = 6A$ and, $I_2 = 5.6A$.



1

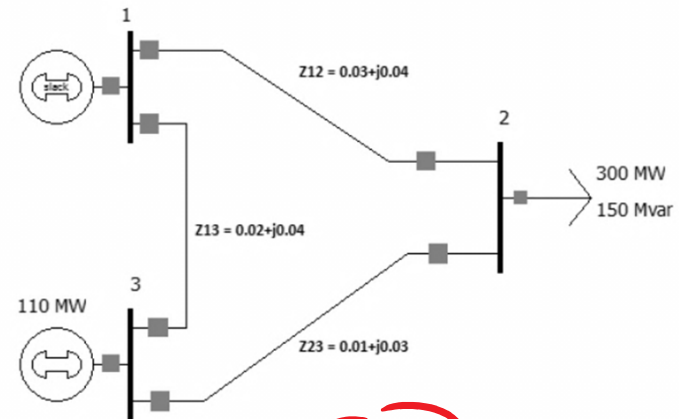No. 2 Find Y bus admittance matrix from fig. below:



2

No. 3

3

PROBLEMS

6.1. A power system network is shown in Figure 6.17. The generators at buses 1 and 2 are represented by their equivalent current sources with their reactances in per unit on a 100-MVA base. The lines are represented by π model where series reactances and shunt reactances are also expressed in per unit on a 100 MVA base. The loads at buses 3 and 4 are expressed in MW and Mvar.

- (a) Assuming a voltage magnitude of 1.0 per unit at buses 3 and 4, convert the loads to per unit impedances. Convert network impedances to admittances and obtain the bus admittance matrix by inspection.
- (b) Use the function $Y = \text{ybus}(zdata)$ to obtain the bus admittance matrix. The function argument $zdata$ is a matrix containing the line bus numbers, resistance and reactance. (See Example 6.1.)

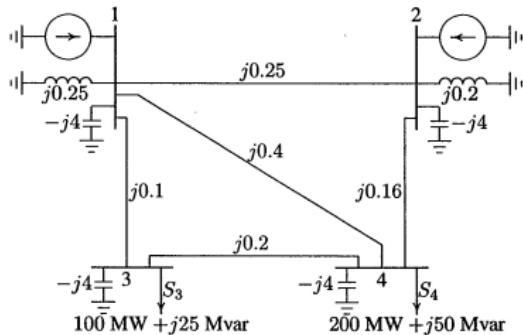


FIGURE 6.17 One-line diagram for Problem 6.1.

No. 4

4

6.2. A power system network is shown in Figure 6.18. The values marked are impedances in per unit on a base of 100 MVA. The currents entering buses 1 and 2 are

$$I_1 = 1.38 - j2.72 \text{ pu}$$

$$I_2 = 0.69 - j1.36 \text{ pu}$$

- (a) Determine the bus admittance matrix by inspection.
- (b) Use the function $Y = \text{ybus}(zdata)$ to obtain the bus admittance matrix. The function argument $zdata$ is a matrix containing the line bus numbers, resistance and reactance. (See Example 6.1.) Write the necessary MATLAB commands to obtain the bus voltages.

